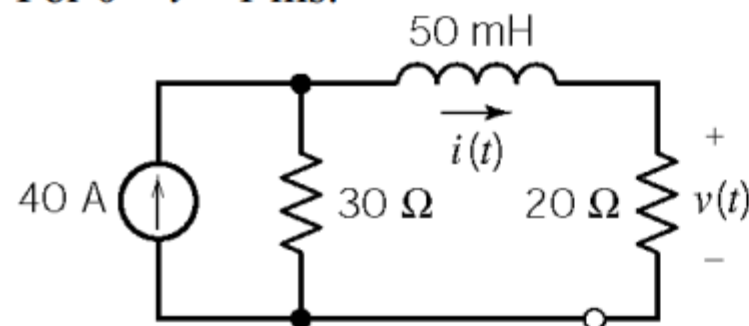


plot $v(t)$ for $0 < t < 0.3$ s.

$$i_s(t) = 40 [u(t) - u(t - t_0)] \text{ A, where } t_0 = 1 \text{ ms.}$$

Assume that the circuit is at steady state before $t = 0$. Then the initial inductor current is $i(0^-) = 0$ A.

For $0 < t < 1$ ms:



The steady state inductor current will be


$$i(\infty) = \lim_{t \rightarrow \infty} i(t) = \frac{30}{30 + 20} (40) = 24 \text{ A}$$

The time constant will be

$$\tau = \frac{50 \times 10^{-3}}{30 + 20} = 10^{-3} = \frac{1}{1000} \text{ s}$$

The inductor current is $i(t) = 24 (1 - e^{-1000t})$ A

For $t > 1 \text{ ms}$

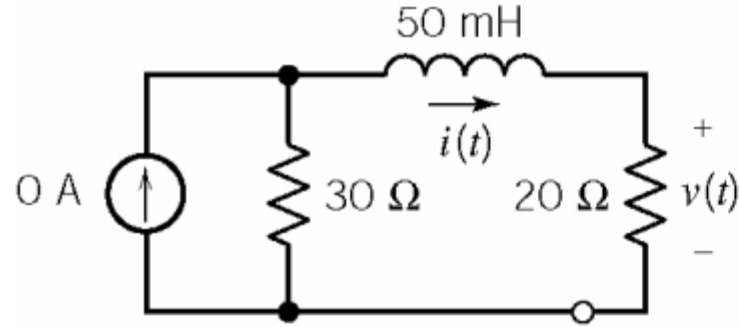


In particular, $i(0.001) = 24(1 - e^{-1}) = 15.2 \text{ A}$

Now the initial current is $i(0.001) = 15.2 \text{ A}$ and the steady state current is 0 A. As before, the time constant is 1 ms. The inductor current is


$$i(t) = 15.2 e^{-1000(t-0.001)} \text{ A}$$

The output voltage is

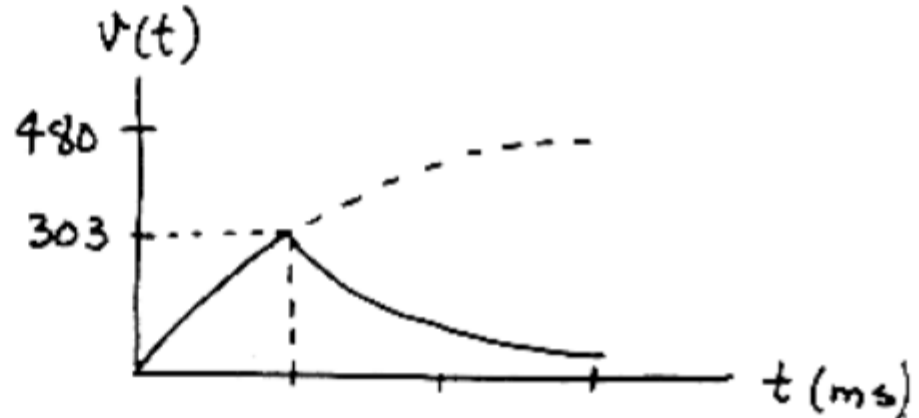
$$v(t) = 20 i(t) = \begin{cases} 480(1 - e^{-1000t}) \text{ V} & t < 1 \text{ ms} \\ 303 e^{-1000(t-0.001)} \text{ V} & t > 1 \text{ ms} \end{cases}$$



$v(t)$ for $t > 0$

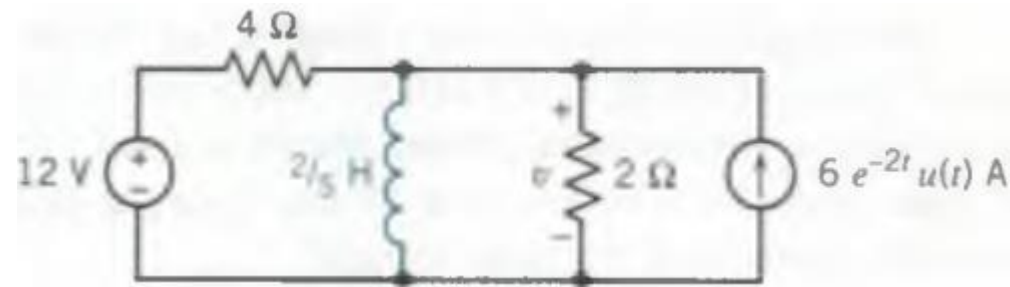

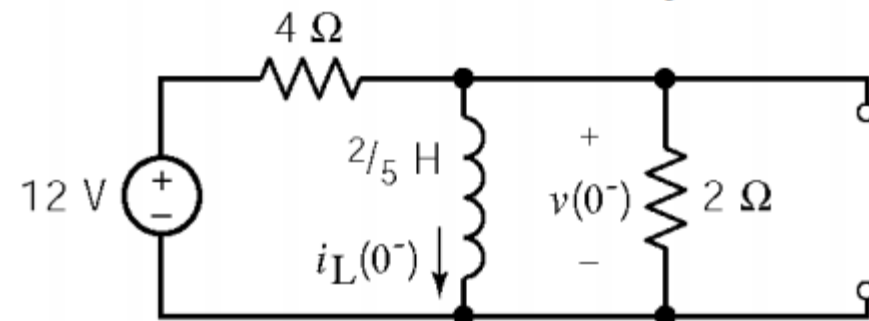Assume that the circuit is at steady state before $t = 0$:



$$i_L(0^+) = i_L(0^-) = \frac{12}{4} = 3\text{ A}$$

After $t = 0$:

$$\text{KCL: } \frac{v(t)-12}{4} + i_L(t) + \frac{v(t)}{2} = 6e^{-2t}$$

$$\text{also: } v(t) = (2/5) \frac{di_L(t)}{dt}$$

$$i_L(t) + \frac{3}{4} \left[(2/5) \frac{di_L(t)}{dt} \right] = 3 + 6e^{-2t}$$

$$\frac{di_L(t)}{dt} + \frac{10}{3} i_L(t) = 10 + 20e^{-2t}$$


$\therefore i_n(t) = Ae^{-(10/3)t}$, try $i_f(t) = B + Ce^{-2t}$, substitute into the differential equation,

and then equating like terms $\Rightarrow B=3, C=15 \Rightarrow i_f(t)=3+15e^{-2t}$


$$\therefore i_L(t) = i_n(t) + i_f(t) = Ae^{-(10/3)t} + 3 + 15e^{-2t}, \quad i_L(0) = 3 = A + 3 + 15 \Rightarrow A = -15$$

$$\therefore i_L(t) = -15e^{-(10/3)t} + 3 + 15e^{-2t}$$

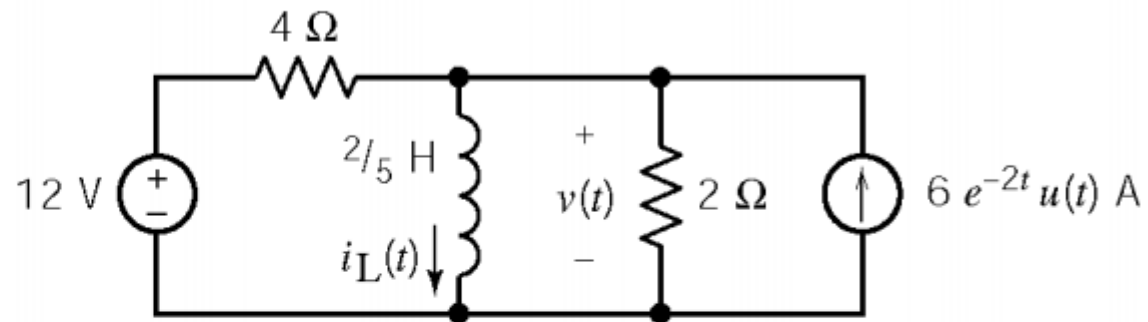
$$\text{Finally, } \underline{v(t) = (2/5) \frac{di_L}{dt} = 20e^{-(10/3)t} - 12e^{-2t} \text{ V}}$$



$v_c(t)$ for $t > 0$

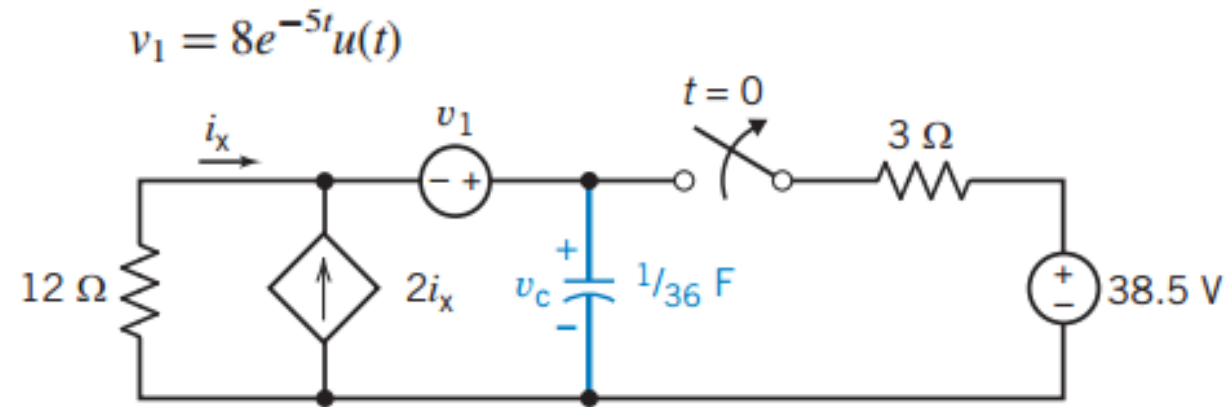

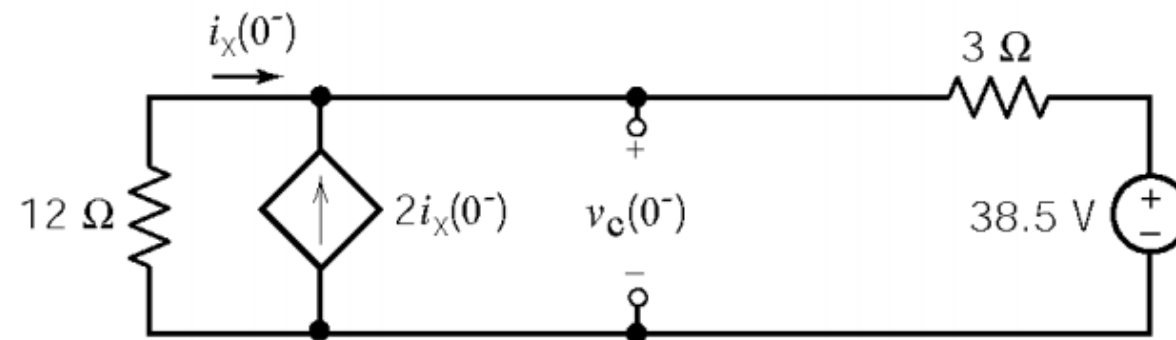
Assume that the circuit is at steady state before $t = 0$:



$$\text{KVL : } 12i_x + 3(3i_x) + 38.5 = 0 \Rightarrow i_x = -1.83 \text{ A}$$

$$\text{Then } \underline{v_c(0^-) = -12i_x = 22 \text{ V} = v_c(0^+)}$$

After $t = 0$:

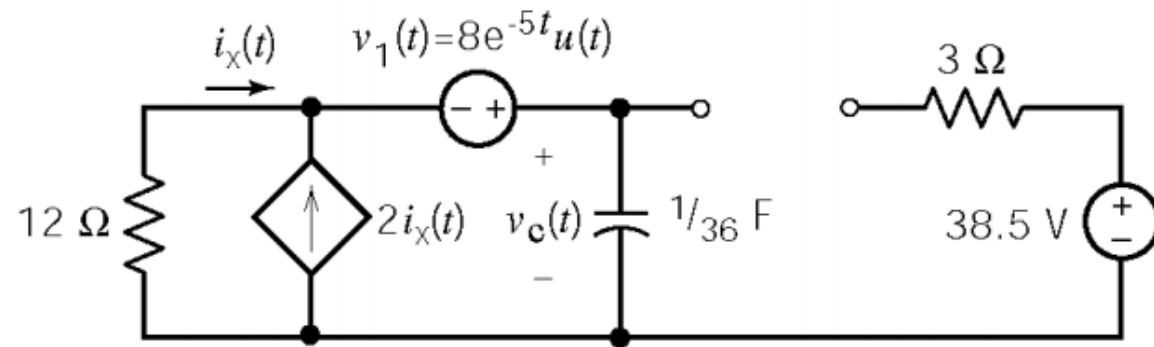

$$\text{KVL : } 12i_x(t) - 8e^{-5t} + v_c(t) = 0$$

$$\text{KCL : } -i_x(t) - 2i_x(t) + (1/36) \frac{dv_c(t)}{dt} = 0 \Rightarrow i_x(t) = \frac{1}{108} \frac{dv_c(t)}{dt}$$

$$\therefore 12 \left[\frac{1}{108} \frac{dv_c(t)}{dt} \right] - 8e^{-5t} + v_c(t) = 0$$

$$\frac{dv_c(t)}{dt} + 9v_c(t) = 72e^{-5t} \Rightarrow v_{cn}(t) = Ae^{-9t}$$


$$\text{Try } v_{cf}(t) = Be^{-5t} \text{ \& substitute into the differential equation } \Rightarrow B = 18$$

$$\therefore v_c(t) = Ae^{-9t} + 18e^{-5t}$$

$$v_c(0) = 22 = A + 18 \Rightarrow A = 4$$


$$\therefore \underline{v_c(t) = 4e^{-9t} + 18e^{-5t} \text{ V}}$$

$v(t)$ for $t > 0$

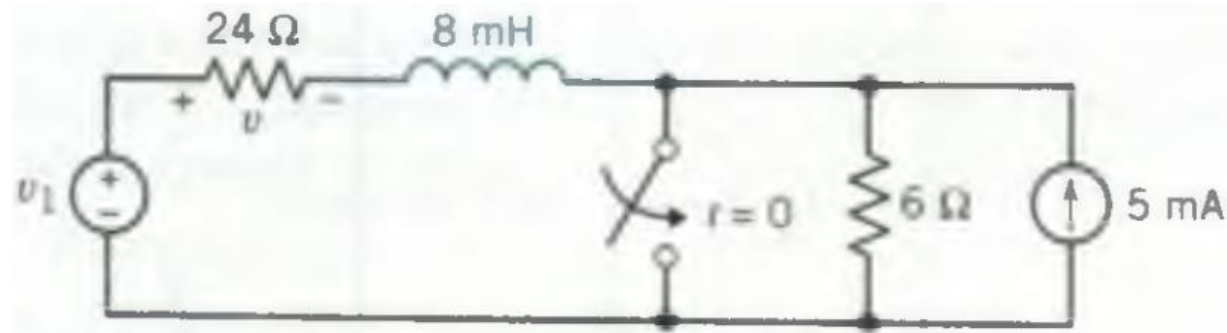

$$v_1 = (25 \sin 4000t)u(t)$$

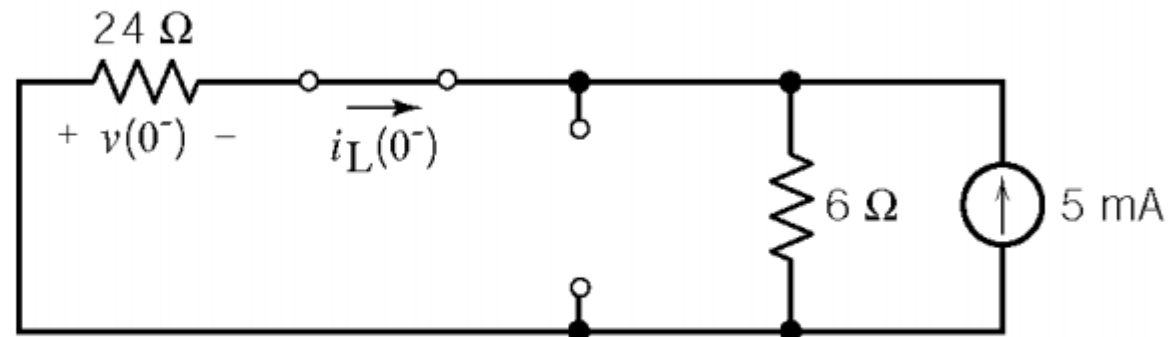Assume that the circuit is at steady state before $t = 0$:




Current division: $i_L(0^-) = -5 \left(\frac{6}{6+24} \right) = -1 \text{ mA}$

After $t = 0$:

$$\text{KVL: } -25 \sin 4000 t + 24 i_L(t) + .008 \frac{di_L(t)}{dt} = 0$$
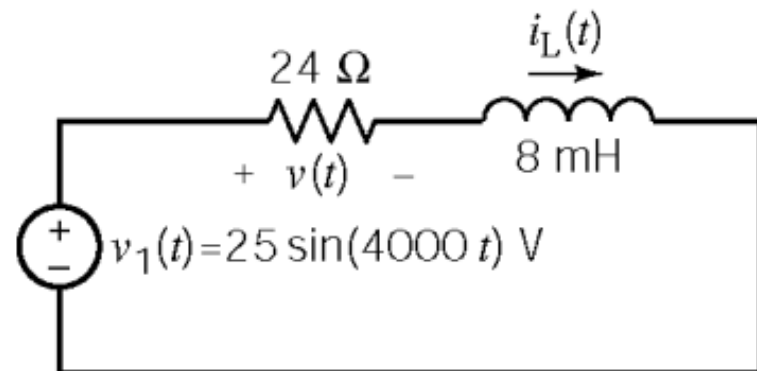
$$\underline{\frac{di_L(t)}{dt} + 3000 i_L(t) = \frac{25}{.008} \sin 4000 t}$$



$i_n(t) = Ae^{-3000t}$, try $i_f(t) = B \cos 4000t + C \sin 4000t$, substitute into the differential equation and equate like terms $\Rightarrow B = -1/2, C = 3/8 \Rightarrow i_f(t) = -0.5 \cos 4000t + 0.375 \sin 4000t$

$$i_L(t) = i_n(t) + i_f(t) = Ae^{-3000t} - 0.5 \cos 4000t + 0.375 \sin 4000t$$

$$i_L(0^+) = i_L(0^-) = -10^{-3} = A - 0.5 \Rightarrow A \cong 0.5$$

$$\therefore i_L(t) = 0.5 e^{-3000t} - 0.5 \cos 4000t + 0.375 \sin 4000t \text{ mA}$$

$$\text{but } v(t) = 24 i_L(t) = 12 e^{-3000t} - 12 \cos 4000t + 9 \sin 4000t \text{ V}$$