



# Computer Architecture

Spring 2020

**Hamed Farbeh**

farbeh@aut.ac.ir

Department of Computer Engineering

Amirkabir University of Technology

**BASIC COMPUTER ORGANIZATION AND DESIGN**




# Outlines

- Instruction Codes
- Computer Registers
- Computer Instructions
- Timing and Control
- Instruction Cycle
- Memory Reference Instructions
- Input-Output and Interrupt
- **Complete Computer Description**
- **Design of Basic Computer**
- **Design of Accumulator Logic**

# COMPLETE COMPUTER DESCRIPTION

Flowchart of Operations

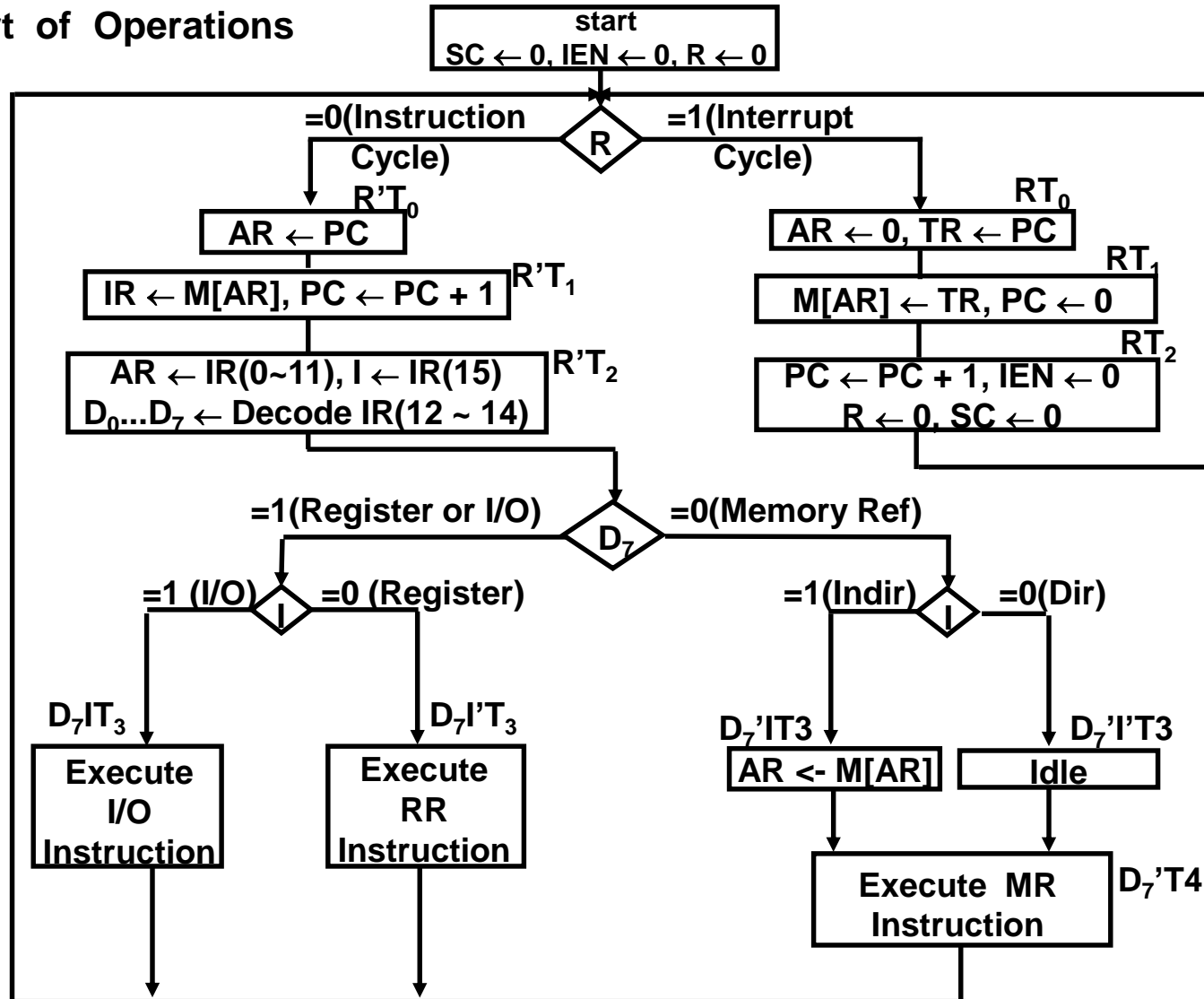

# COMPLETE COMPUTER DESCRIPTION

## Microoperations

Fetch	$R'T_0:$	$AR \leftarrow PC$
	$R'T_1:$	$IR \leftarrow M[AR], PC \leftarrow PC + 1$
Decode	$R'T_2:$	$D_0, \dots, D_7 \leftarrow \text{Decode } IR(12 \sim 14),$ $AR \leftarrow IR(0 \sim 11), I \leftarrow IR(15)$
Indirect	$D_7'IT_3:$	$AR \leftarrow M[AR]$
Interrupt	$T_0'T_1'T_2'(IEN)(FGI + FGO):$	$R \leftarrow 1$
	$RT_0:$	$AR \leftarrow 0, TR \leftarrow PC$
	$RT_1:$	$M[AR] \leftarrow TR, PC \leftarrow 0$
	$RT_2:$	$PC \leftarrow PC + 1, IEN \leftarrow 0, R \leftarrow 0, SC \leftarrow 0$
Memory-Reference		
AND	$D_0T_4:$	$DR \leftarrow M[AR]$
	$D_0T_5:$	$AC \leftarrow AC \wedge DR, SC \leftarrow 0$
ADD	$D_1T_4:$	$DR \leftarrow M[AR]$
	$D_1T_5:$	$AC \leftarrow AC + DR, E \leftarrow C_{out}, SC \leftarrow 0$
LDA	$D_2T_4:$	$DR \leftarrow M[AR]$
	$D_2T_5:$	$AC \leftarrow DR, SC \leftarrow 0$
STA	$D_3T_4:$	$M[AR] \leftarrow AC, SC \leftarrow 0$
BUN	$D_4T_4:$	$PC \leftarrow AR, SC \leftarrow 0$
BSA	$D_5T_4:$	$M[AR] \leftarrow PC, AR \leftarrow AR + 1$
	$D_5T_5:$	$PC \leftarrow AR, SC \leftarrow 0$
ISZ	$D_6T_4:$	$DR \leftarrow M[AR]$
	$D_6T_5:$	$DR \leftarrow DR + 1$
	$D_6T_6:$	$M[AR] \leftarrow DR, \text{ if } (DR=0) \text{ then } (PC \leftarrow PC + 1),$ $SC \leftarrow 0$

# COMPLETE COMPUTER DESCRIPTION

## Microoperations

### Register-Reference

	$D_7I'T_3 = r$	(Common to all register-reference instr)
	$IR(i) = B_i$	( $i = 0, 1, 2, \dots, 11$ )
	$r:$	$SC \leftarrow 0$
CLA	$rB_{11}:$	$AC \leftarrow 0$
CLE	$rB_{10}:$	$E \leftarrow 0$
CMA	$rB_9:$	$AC \leftarrow AC'$
CME	$rB_8:$	$E \leftarrow E'$
CIR	$rB_7:$	$AC \leftarrow shr AC, AC(15) \leftarrow E, E \leftarrow AC(0)$
CIL	$rB_6:$	$AC \leftarrow shl AC, AC(0) \leftarrow E, E \leftarrow AC(15)$
INC	$rB_5:$	$AC \leftarrow AC + 1$
SPA	$rB_4:$	If( $AC(15) = 0$ ) then ( $PC \leftarrow PC + 1$ )
SNA	$rB_3:$	If( $AC(15) = 1$ ) then ( $PC \leftarrow PC + 1$ )
SZA	$rB_2:$	If( $AC = 0$ ) then ( $PC \leftarrow PC + 1$ )
SZE	$rB_1:$	If( $E = 0$ ) then ( $PC \leftarrow PC + 1$ )
HLT	$rB_0:$	$S \leftarrow 0$

### Input-Output

	$D_7IT_3 = p$	(Common to all input-output instructions)
	$IR(i) = B_i$	( $i = 6, 7, 8, 9, 10, 11$ )
	$p:$	$SC \leftarrow 0$
INP	$pB_{11}:$	$AC(0-7) \leftarrow INPR, FGI \leftarrow 0$
OUT	$pB_{10}:$	$OUTR \leftarrow AC(0-7), FGO \leftarrow 0$
SKI	$pB_9:$	If( $FGI = 1$ ) then ( $PC \leftarrow PC + 1$ )
SKO	$pB_8:$	If( $FGO = 1$ ) then ( $PC \leftarrow PC + 1$ )
ION	$pB_7:$	$IEN \leftarrow 1$
IOF	$pB_6:$	$IEN \leftarrow 0$

# DESIGN OF BASIC COMPUTER (BC)

## Hardware Components of BC

A memory unit: 4096 x 16.

Registers:

AR, PC, DR, AC, IR, TR, OUTR, INPR, and SC

Flip-Flops(Status):

I, S, E, R, IEN, FGI, and FGO

Decoders: a 3x8 Opcode decoder  
a 4x16 timing decoder

Common bus: 16 bits

Control logic gates:

Adder and Logic circuit: Connected to AC

## Control Logic Gates

- Input Controls of the nine registers
- Read and Write Controls of memory
- Set, Clear, or Complement Controls of the flip-flops
- $S_2, S_1, S_0$  Controls to select a register for the bus
- AC, and Adder and Logic circuit

# CONTROL OF REGISTERS AND MEMORY


## Address Register; AR

Scan all of the register transfer statements that change the content of AR:

$R'T_0$ :	$AR \leftarrow PC$	$LD(AR)$
$R'T_2$ :	$AR \leftarrow IR(0-11)$	$LD(AR)$
$D'_7IT_3$ :	$AR \leftarrow M[AR]$	$LD(AR)$
$RT_0$ :	$AR \leftarrow 0$	$CLR(AR)$
$D_5T_4$ :	$AR \leftarrow AR + 1$	$INR(AR)$



 $LD(AR) = R'T_0 + R'T_2 + D'_7IT_3$
$CLR(AR) = R'T_0$
$INR(AR) = D_5T_4$



# CONTROL OF FLAGS


## IEN: Interrupt Enable Flag

$pB_7$ :  $IEN \leftarrow 1$  (I/O Instruction)

$pB_6$ :  $IEN \leftarrow 0$  (I/O Instruction)


$RT_2$ :  $IEN \leftarrow 0$  (Interrupt)

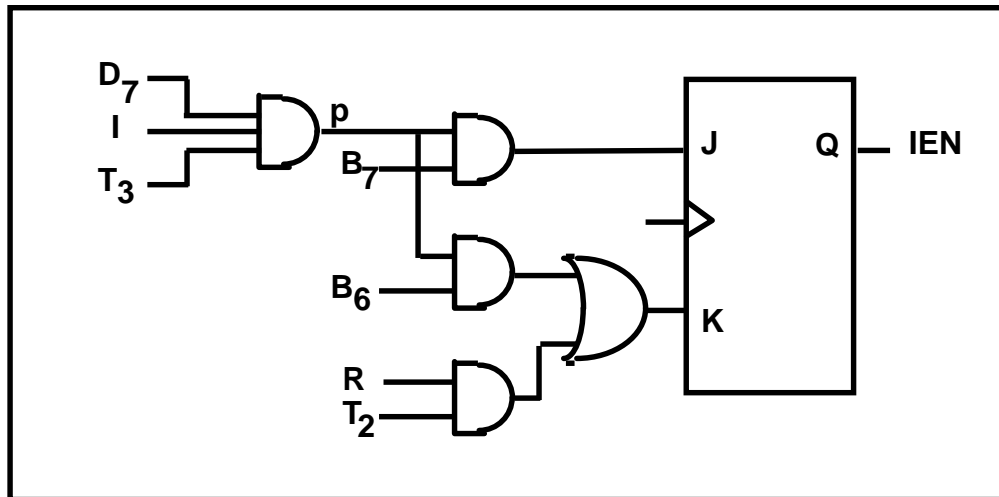$p = D_7IT_3$  (Input/Output Instruction)





# CONTROL OF COMMON BUS

 

$x_1$	$x_2$	$x_3$	$x_4$	$x_5$	$x_6$	$x_7$	$S_2$	$S_1$	$S_0$	selected register
0	0	0	0	0	0	0	0	0	0	none
1	0	0	0	0	0	0	0	0	1	AR
0	1	0	0	0	0	0	0	1	0	PC
0	0	1	0	0	0	0	0	1	1	DR
0	0	0	1	0	0	0	1	0	0	AC
0	0	0	0	1	0	0	1	0	1	IR
0	0	0	0	0	1	0	1	1	0	TR
0	0	0	0	0	0	1	1	1	1	Memory

For AR


$D_4T_4: PC \leftarrow AR$   
 $D_5T_5: PC \leftarrow AR$



$$x_1 = D_4T_4 + D_5T_5$$

# DESIGN OF ACCUMULATOR LOGIC

## Circuits associated with AC

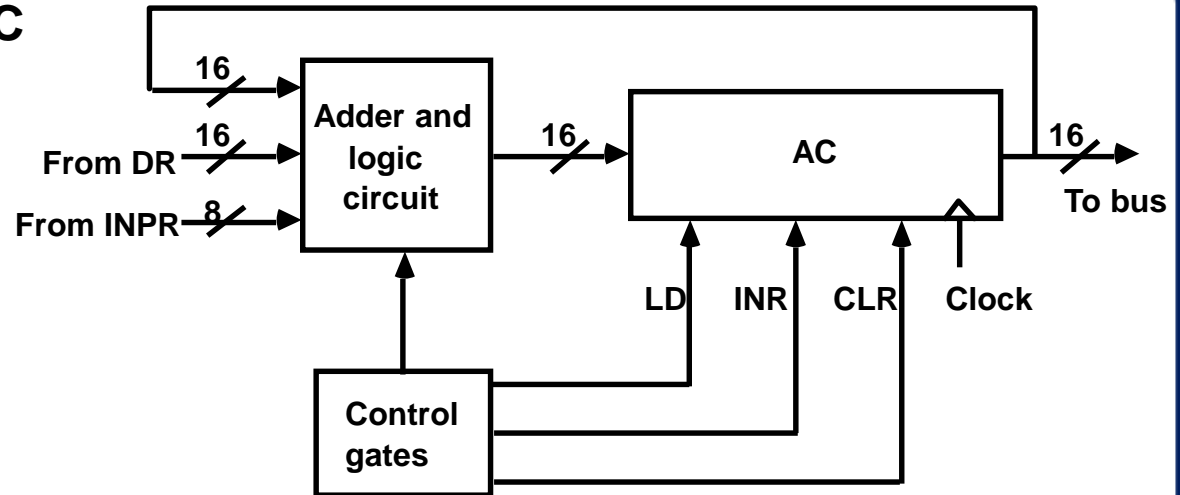


## All the statements that change the content of AC

$D_0T_5:$	$AC \leftarrow AC \wedge DR$	AND with DR
$D_1T_5:$	$AC \leftarrow AC + DR$	Add with DR
$D_2T_5:$	$AC \leftarrow DR$	Transfer from DR
$pB_{11}:$	$AC(0-7) \leftarrow INPR$	Transfer from INPR
$rB_9:$	$AC \leftarrow AC'$	Complement
$rB_7:$	$AC \leftarrow shr\ AC, AC(15) \leftarrow E$	Shift right
$rB_6:$	$AC \leftarrow shl\ AC, AC(0) \leftarrow E$	Shift left
$rB_{11}:$	$AC \leftarrow 0$	Clear
$rB_5:$	$AC \leftarrow AC + 1$	Increment

 
# CONTROL OF AC REGISTER

Gate structures for controlling the LD, INR, and CLR of AC



# ALU (ADDER AND LOGIC CIRCUIT)

## One stage of Adder and Logic circuit

 

# End of Chapter 5 (Mano)