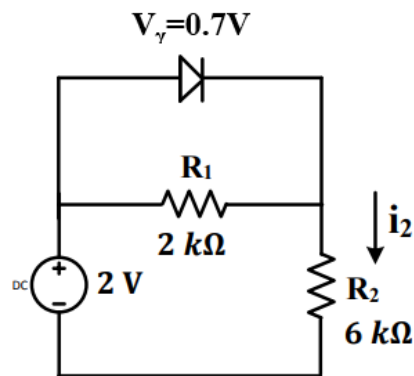



## جواب تمرینات سری ششم

-۲


شکل (الف)



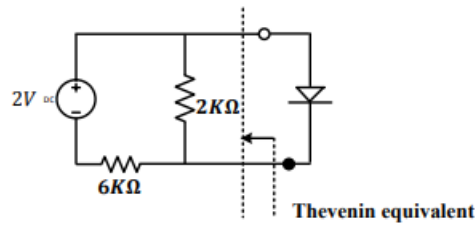
Soln. The given circuit can be redrawn as



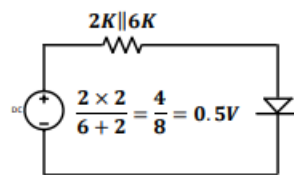This circuit can be further simplified using Thevenins theorem



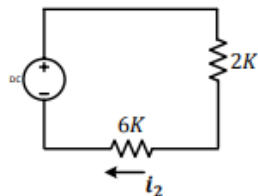Voltage across diode is 0.5V thus the diode is OFF. The circuit reduces to




The current through 6 K

$$i_2 = \frac{2}{2K + 6K} = \frac{2}{8K} = 0.25 \text{ mA}$$

Answer: 0.25 mA

شكل (ب)

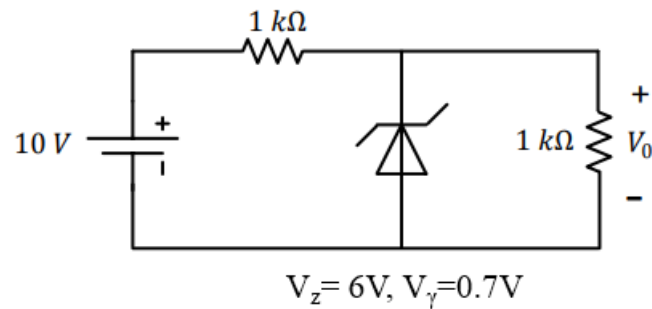


**Zener voltage = 6 V**

**Zener diode is reverse biased during its operation. Here with the applied voltage, the voltage across the Zener diode is**

$$V_0 = \frac{1\text{ k}\Omega}{1\text{ k} + 1\text{ k}\Omega} \times 10V = 5V$$


**Diode will be reverse biased but not in the Zener region, so open circuited.**

**Answer Thus,  $V_0 = 5V$**

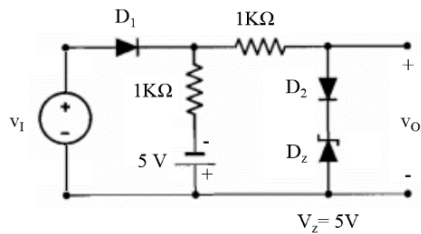

-3

$D_1, D_2 : off$

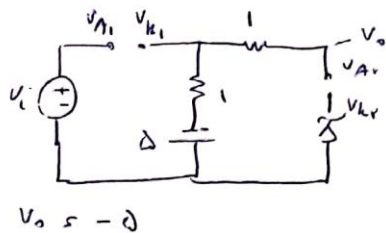


$$v_o \leq -\Delta$$

$$(1) \quad v_i < -\Delta \rightarrow v_o = -\Delta$$

در صورتی که ولتاژ ورودی کمتر از ولتاژ معکوس باشد

$$\begin{aligned} v_{A_1} - v_{K_1} &< 0 & v_{A_1} - v_{K_2} &< 0 \\ v_i - (-\Delta) &< 0 & -\Delta - v_o &< 0 \\ v_i &< -\Delta & \text{شرایط برقرار} \end{aligned}$$

$D_1 : on, D_2 : off$

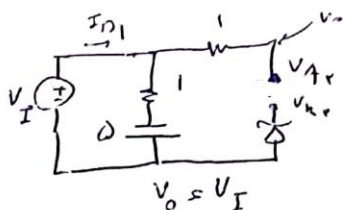


$$v_o = v_i$$

$$\begin{aligned} v_{A_1} - v_{K_2} &< 0 \\ v_i - v_o &< 0 \\ v_i - \Delta &< 0 & v_i &< \Delta \end{aligned}$$

$$\begin{aligned} I_{D_1} &> 0 \\ I_{D_1} = \frac{v_i + \Delta}{1} &> 0 & v_i &> -\Delta \end{aligned}$$

$$(2) \quad -\Delta < v_i < \Delta \quad v_o = v_i$$

$D_1 : off, D_2 : on$

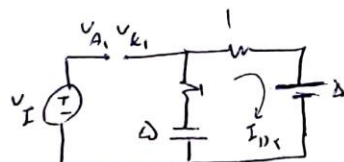

$$I_{D_2} = \frac{-v_o - \Delta}{1} < 0$$

فرض بر اینست که \$D\_2\$ در حال روشن شدن است

$D_1 : on, D_2 : on$


$$v_o = \Delta$$




$$I_{D_2} = \frac{v_i - \Delta}{1} > 0 \quad v_i > \Delta$$

$$I_{D_1} = \frac{v_i + \Delta}{1} + \frac{v_i - \Delta}{1} > 0 \quad v_i > 0$$
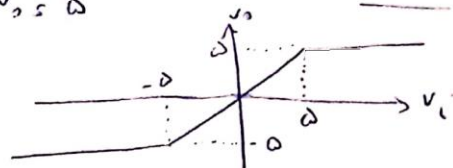
$$(3) \quad v_i > \Delta \quad v_o = \Delta$$



شکل (الف)

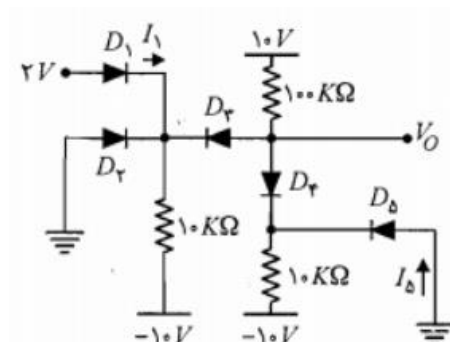

با توجه به مدار داریم:  $D_1: \text{ON} \quad D_2: \text{OFF} \quad D_3: \text{OFF} \quad D_4: \text{ON} \quad D_\Delta: \text{ON}$


$$I_1 = \frac{2V - (-10V)}{10K\Omega} = 1/2 \text{ mA}$$

و چون  $D_2$  و  $D_3$  روشن می‌باشند پس  $V_o = 0V$  می‌باشد.

$$\text{KCL در نقطه A: } \frac{V_o - 10V}{100K\Omega} - I_\Delta + \frac{V_o - (-10V)}{10K\Omega} = 0$$


$$V_o = 0V \rightarrow \frac{-10}{100} - I_\Delta + \frac{10}{10} = 0 \rightarrow I_\Delta = 1 - 0/1 = 0/9 \text{ mA}$$

شکل (ب)

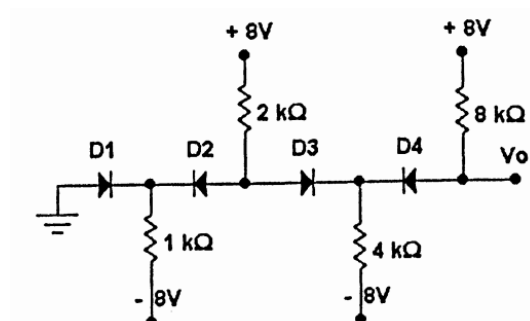

فردی در این مدار:

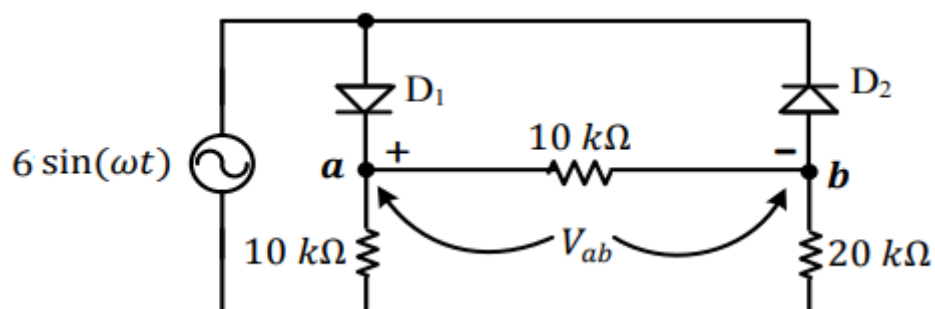
$V_o = 0$   
 $I_{D2} = \frac{10-0}{1k} = 10 \text{ mA} > 0$   
 $I_{D3} = -I_{D2} + \frac{0+10}{2k} = 10 \text{ mA} > 0$   
 $I_{D4} = I_{D2} + I_{D3} + \frac{0-10}{2k} = 0$   
 $I_{D5} = I_{D4} - 10 = -10 \text{ mA} < 0$   
 $I_{D6} = I_{D5} + \frac{0+10}{4k} = 10 \text{ mA} > 0$



**D<sub>1</sub> is Forward biased and**

**D<sub>2</sub> is Reverse biased**

The circuit reduces to

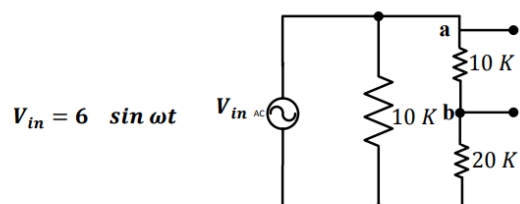

$$V_{ab} = \frac{10 K}{10 K + 20 K} \cdot V_{in}$$



$$= \frac{V_{in}}{3} = \frac{6 \sin \omega t}{3} = 2 \sin \omega t$$


**D<sub>1</sub> is Reverse biased**

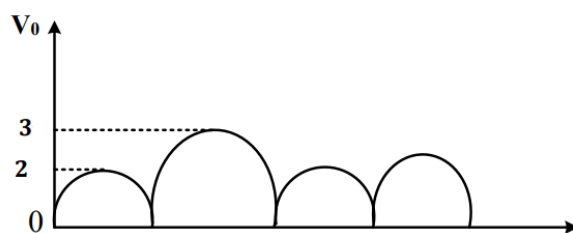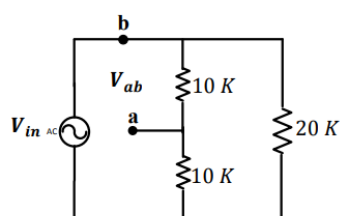**D<sub>2</sub> is Forward biased**


$$V_{ab} = \frac{10 K}{10 K + 10 K} \cdot V_{in} = V_{in} / 2$$

$$= \frac{6 \sin \omega t}{2} = 3 \sin \omega t$$



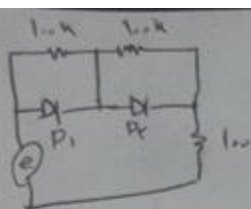

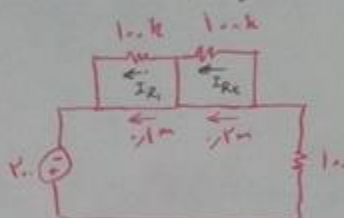هین در صورت سوال صافتر و کمتر معکوس دیوها  
خفایه شده، یعنی دیوها معکوس یا پس شده اند  
و همین اشیاء معکوس از دیوها منفرجه



$$\text{KVL} \quad 2 = 10^4 I_{R1} + 10^4 I_{R2} + 100 (I_{R1} + I_{R2}) \quad (1)$$

$$\text{KCL} \quad I_{R1} + I_{R2} = I_{R1} + I_{R2} \quad I_{R1} = I_{R2} + I_{R2} \quad (2)$$

$$2 = 10^4 (I_{R1} + I_{R2}) + 10^4 I_{R2} + 100 (I_{R1} + I_{R2})$$

$$2 = 10 + 10^4 I_{R2} + 100 + 100 I_{R2}$$

$$189,98 = 10^4 I_{R2}$$

$$I_{R2} = 0,01899 \text{ mA}$$

$$I_{R1} = 0,01 + 0,01899 = 0,02899 \text{ mA}$$

$$V_{R1} = 10^4 \times I_{R1} = 0,2899 \text{ V}$$

$$V_{R2} = 10^4 \times I_{R2} = 0,1899 \text{ V}$$